

Output Current Sensing

for the MC35XS3400 eXtreme Switch Device

1 Introduction

This application note relates to the output current sensing of 3rd generation Quad 35 mΩ device.

This application note presents the current sensing accuracy and the practical implementation of a calibration procedure to improve it.

Contents

1 Introduction	1
2 Scope	2
3 Selectable Current Sensing Overview	3
4 Calibration Practice	4
5 MCU Current Sense Monitoring	6
5.1 Current Sense Response Time	6
5.2 Synchronization of MCU Analog-to-Digital Conversion	7

2 Scope

This device is designed for low-voltage automotive lighting applications. Its four low $R_{DS(ON)}$ MOSFETs can control four separate 28 W bulbs or LEDs, or other type of loads.

Programming, control, and diagnostics are accomplished using a 16-bit SPI interface. The programmable slew rate of each output makes it easier to satisfy electromagnetic compatibility (EMC) requirements. Additionally, each output can be controlled by an internal PWM modulated clock signal instead of an external clock.

This IC's diagnostic features are essential to ensuring its safety, and they provide the microcontroller (MCU) with highly accurate and timely information regarding the status each lamp. Digital diagnostics are reported to the MCU using a SPI communication, and an analog feedback signal provides current and temperature data to one of the MCU's A/D inputs. For example, a current proportional to the selected output's load current is provided by the device's CSNS pin. So, the current of a bulb can be fully supervised in real time by the MCU. The purpose of this application note is to quantify the current sensing tolerance with and without calibration at the module level.

[Figure 1](#) shows a typical application diagram using this type of quad high side device.

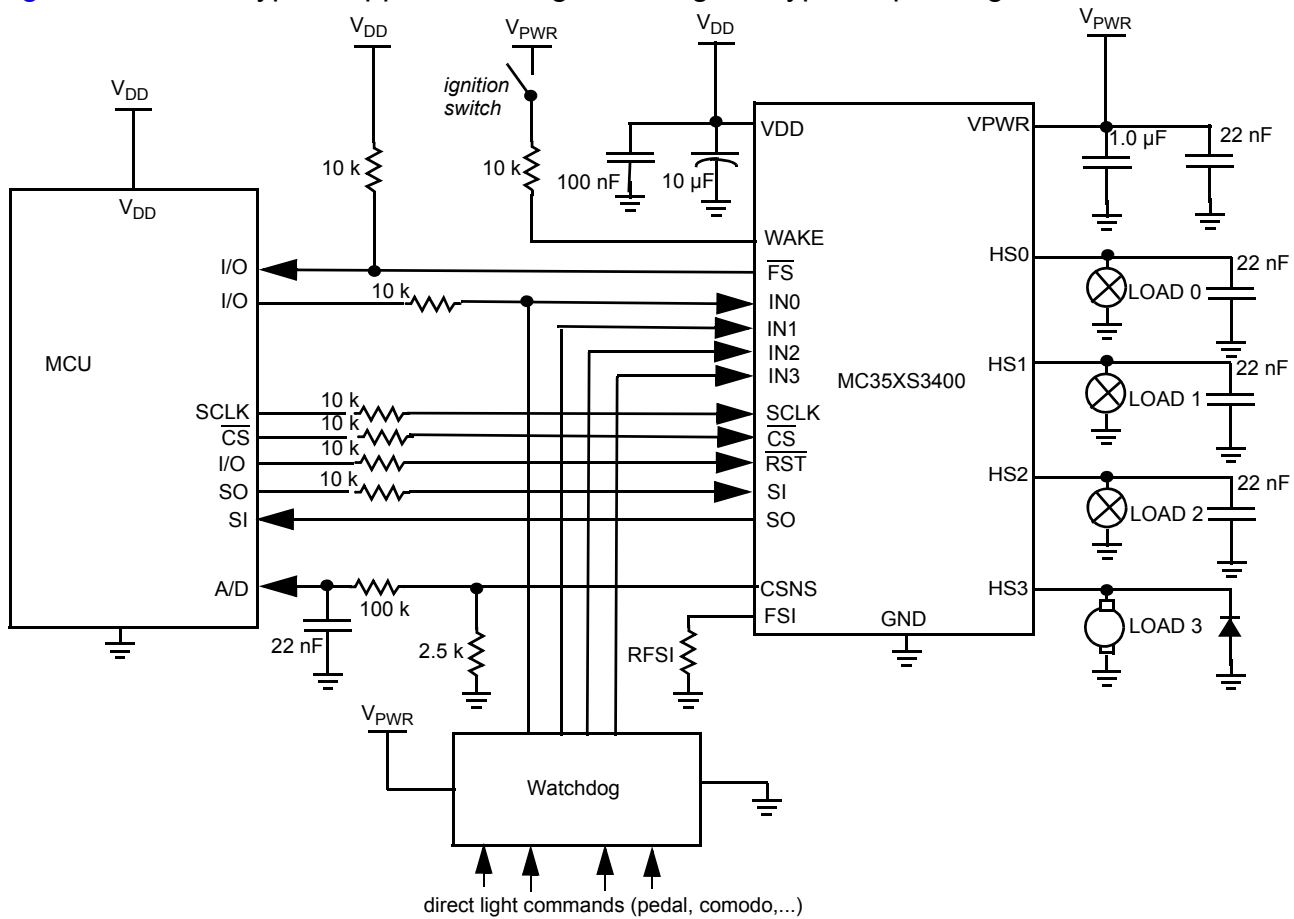


Figure 1. Typical Application Diagram

3 Selectable Current Sensing Overview

The current sensing ratio can be adjusted according to the intended lamp wattage and operation mode. For example, the CSR0 and CSR1 ratios can be used to monitor the lamp current respectively during the steady state and in the inrush phase.

[Figure 2](#) presents the appropriate current sense ratio.

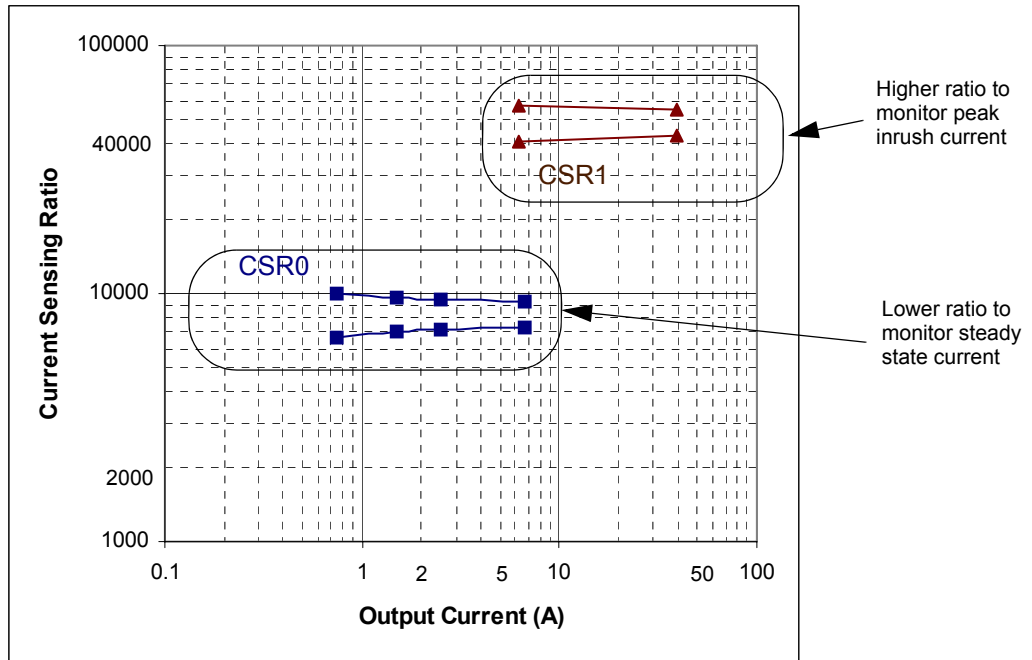


Figure 2. Current Sense Ratio in Function to Output Current Range

[Figure 3](#) describes the accuracy of the current sense as a function of the output current for the ambient temperature range [-40°C, 125°C] and battery voltage range [6.0 V, 20 V].

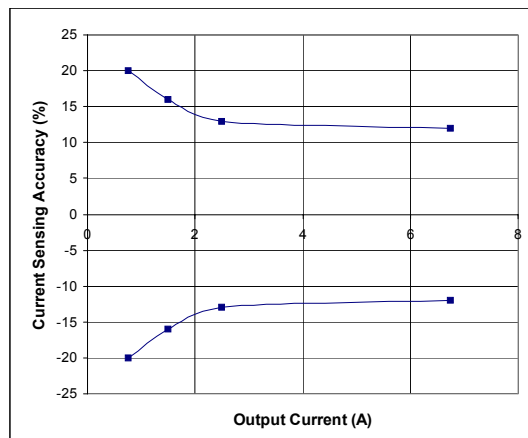


Figure 3. CSR0 Current Sense Variation

Based on statistical data analysis performed on two production lots (initial testing only), the effect of each contributor has been demonstrated for:

1. device to device deviation due to manufacturing
2. ambient temperature drift
3. battery voltage range

4 Calibration Practice

Calibration at a single point removes the device to device error contribution for that condition. Multiple calibration points remove variation at other conditions.

An experiment was done on low output current values. The relative CSR0 deviation based on only two calibration points per output was performed on two production lots. Between each calibration point, the linear regression was used for measuring CSNS analog current feedback high precision. [Figure 4](#) and [Figure 5](#) present the statistical results at 5 Sigma for battery voltage range from 9.0 to 16 V.

[Table 1](#) summarizes the accuracy at 1.0 A output current. There is a possibility of using the analog temperature feedback feature of the device to distinguish low a temperature range (-40°C to +25°C) and a high temperature range (+25°C to +125°C).


Table 1. Current Recopy Accuracy at 1.0 A Output Current

Without Calibration	With Calibration at 85°C only		
	Two Calibration Points		
from -40degC to 125degC	at -40degC	at 25degC	at 125degC
+17%, -17%	+10%, -3.0%	+6.0%, -2.4%	+3.0%, -3.5%


Note: Those results do not take into account the errors in the MCU and external sense resistor connected to the CSNS terminal.

Two calibration points at 85°C were 0.7 A and 2.0 A for $V_{PWR} = 13.5\text{ V}$:


$T_A = -40^\circ\text{C}$

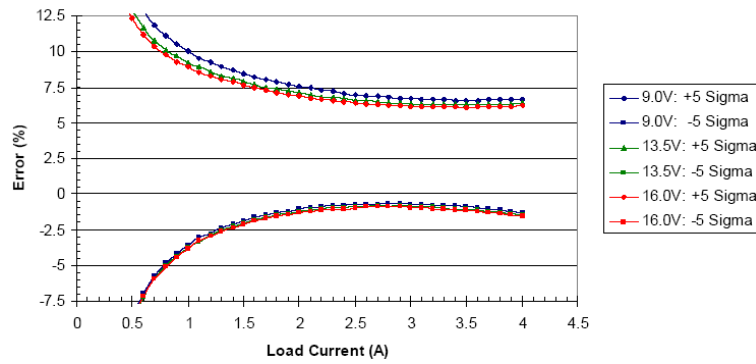

$T_A = 25^\circ\text{C}$

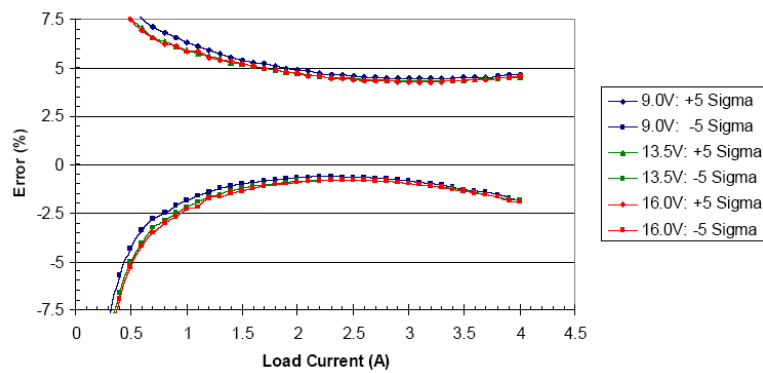

$T_A = 85^\circ\text{C}$

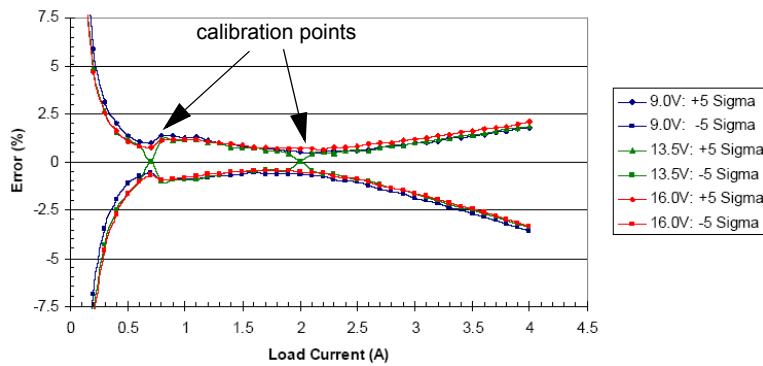

$T_A = 125^\circ\text{C}$

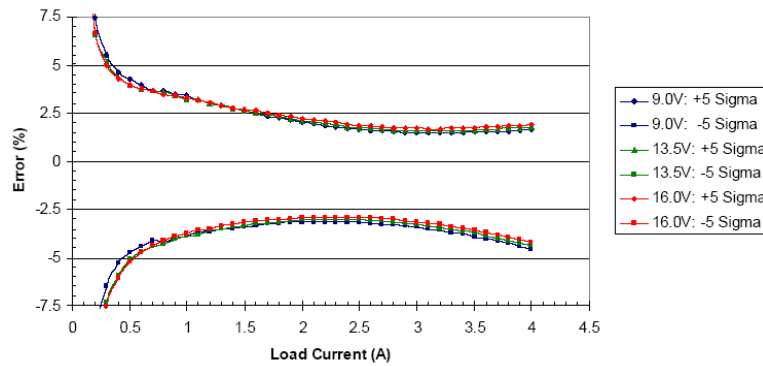


Figure 4. Calibrated CSR0 Current Sense Variation

5 MCU Current Sense Monitoring

5.1 Current Sense Response Time

Figure 5 describes the dynamic response of the current sensing function:

- 140 μ sec. typical ($t_{DLY(ON)} + t_{CSNS(VAL)}$) after the turn-on command coming from the IN pin or SPI command, the current recopy is within +/-5% of the final value, whatever the battery voltage and the output current values,
- The CSNS output typically lags 5.0 μ sec ($t_{CSNS(SET)}$) behind the actual selected output current.

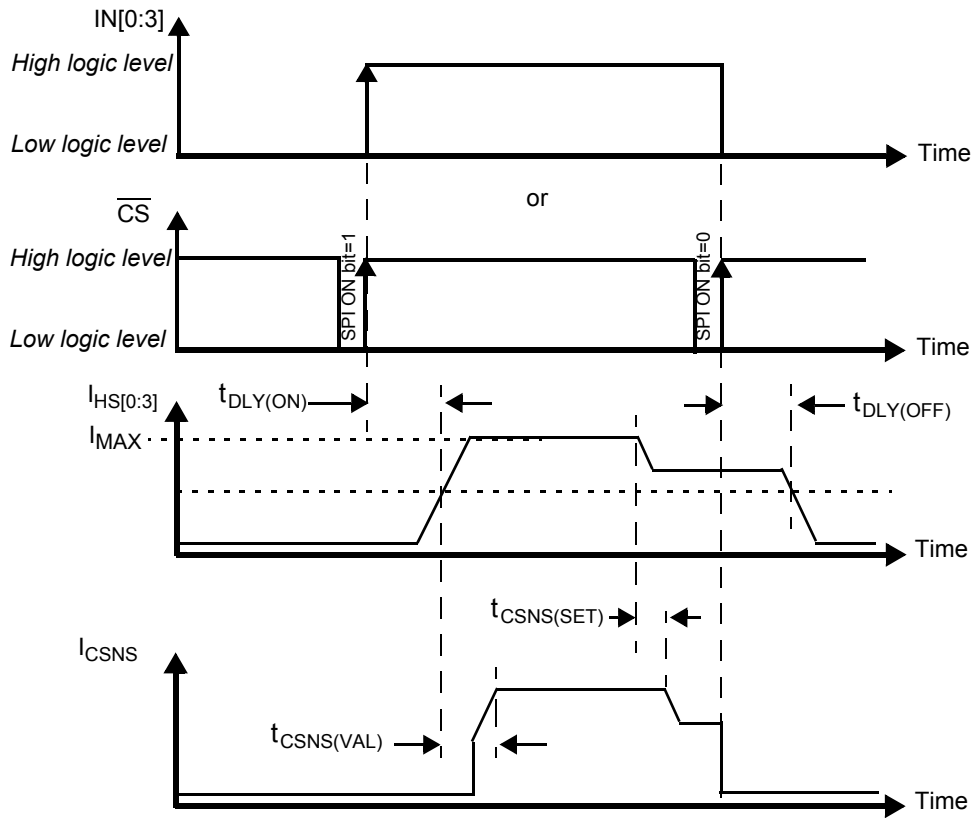


Figure 5. Current Sensing Time Delays

The current recopy transient response fulfils to 3.0% duty cycle of 200 Hz PWM output switching, with the default slew rate (4.0% duty-cycle for 400Hz PWM frequency with fast slew-rate selected).

5.2 Synchronization of MCU Analog-to-Digital Conversion

In many medium and high end microcontrollers, as in the Freescale's MC9S12XE, the Analog-to-Digital (A/D) converter includes features combining interrupt generation and data acquisition.

Either an external control signal (ETRIGx) or the CSNS signal may be used to trigger the A/D conversion, by first generating an interrupt and then sampling the analog value after the defined delay time. By using this feature, polling of the analog value at the CSNS pin can be avoided, thus alleviating microcontroller overhead, and reducing average power consumption.

How to Reach Us:

Home Page:

www.freescale.com

Web Support:

<http://www.freescale.com/support>

USA/Europe or Locations Not Listed:

Freescale Semiconductor, Inc.
Technical Information Center, EL516
2100 East Elliot Road
Tempe, Arizona 85284
+1-800-521-6274 or +1-480-768-2130
www.freescale.com/support

Europe, Middle East, and Africa:

Freescale Halbleiter Deutschland GmbH
Technical Information Center
Schatzbogen 7
81829 Muenchen, Germany
+44 1296 380 456 (English)
+46 8 52200080 (English)
+49 89 92103 559 (German)
+33 1 69 35 48 48 (French)
www.freescale.com/support

Japan:

Freescale Semiconductor Japan Ltd.
Headquarters
ARCO Tower 15F
1-8-1, Shimo-Meguro, Meguro-ku,
Tokyo 153-0064
Japan
0120 191014 or +81 3 5437 9125
support.japan@freescale.com

Asia/Pacific:

Freescale Semiconductor China Ltd.
Exchange Building 23F
No. 118 Jianguo Road
Chaoyang District
Beijing 100022
China
+86 10 5879 8000
support.asia@freescale.com

For Literature Requests Only:

Freescale Semiconductor Literature Distribution Center
P.O. Box 5405
Denver, Colorado 80217
1-800-441-2447 or 303-675-2140
Fax: 303-675-2150
LDCForFreescaleSemiconductor@hibbertgroup.com

Information in this document is provided solely to enable system and software implementers to use Freescale Semiconductor products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits or integrated circuits based on the information in this document.

Freescale Semiconductor reserves the right to make changes without further notice to any products herein. Freescale Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Freescale Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters that may be provided in Freescale Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals", must be validated for each customer application by customer's technical experts. Freescale Semiconductor does not convey any license under its patent rights nor the rights of others. Freescale Semiconductor products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Freescale Semiconductor product could create a situation where personal injury or death may occur. Should Buyer purchase or use Freescale Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold Freescale Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Freescale Semiconductor was negligent regarding the design or manufacture of the part.

Freescale™ and the Freescale logo are trademarks of Freescale Semiconductor, Inc. All other product or service names are the property of their respective owners.

© Freescale Semiconductor, Inc., 2009. All rights reserved.